

ZL 12/8/22

For my final Project I will make a bot that follows the brightest light's source. I will be building my circuitry onto an available chassis that has 2 12V DC motors connected to tracks. The first step is to design the Sensor Controls. I will use two light sensors to determine Left and Right Controls. The light sensor has a Linear Resistance the brighter a light shines on it. With a voltage divider between the sensor and a Resistor and the sensor on top then the brighter the light the higher the voltage output. We can compare each sensor output to each other and a set threshold above ambient light. We can combine the OP-AMP comparator outputs to create three output signals, "Left" sensor above threshold AND brighter than "Right" for "Left" Control, "Right" sensor above threshold AND brighter than "Left" for "Right" Control. When Left AND Right sensors are above the threshold will be the "Forward" output. Next I will design logic to control two H-Bridge drivers to control each motor. One will drive in Forward while the other in Reverse to turn one direction and vice versa to turn the other way. Lastly, I will need to design logic for the "forward" signal to drive both motors forward. In addition to driving the motors we want Indicator lights for Turning Left, Turning Right, and Move forward. Finally, I want to select between three modes: Indicator; where the motors don't activate but the LED Indicators show desired operation, Turning; where the lights indicate and the motors turn the robot but won't advance forward, and Drive; where the lights indicate, motors turn, and the bot moves forward toward the light.

• First let's take a closer look at the functionality of the light sensor (Photo Resistor)


GMQ-5506

The 5506 is a PhotoResistor where its Resistance is dependent on the amount of light present. A PhotoResistor's Resistance decreases when light increases.

5506 Max Ratings

$V_{max} = 100V$ Photo Resistance (10 Lux) $\approx 2K6K \Omega$
 $P_{max} = 90mW$ Dark Resistance = $150K \Omega$
 Ambient Temp = $-30^{\circ}C - +70^{\circ}C$
 Response Time: Rise = $30ms$; Decay = $40ms$

Photo Resistor Schematic Symbol

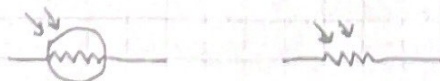

Lab 7: Projects


22.12/17/22

We will start by measuring the Resistance of the 5506 in different conditions.

- Ambient Light @ 4m dark $\approx 2.5k\Omega$
- Flashlight: 6" distance $\approx 500\Omega$; up close $\approx 60\Omega$
- Thumb Covering $\approx 18k\Omega$


To sense light we will make a voltage divider with the PhotoResistor and a $2.2k\Omega$ Resistor. As the PhotoResistor is $\approx 2.5k$ at Ambient, the Voltage Split will be $\approx 50/50$ in ambient light. As the Light increases the Voltage on the output will increase.

Figure 7.1: Left and Right Light Sensors

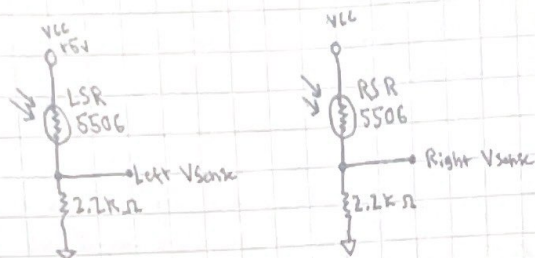

Then we can compare these two signals to each other and adjust a Variable Threshold. We will create 3 signals from these outputs: Left, Right, and Both. Indicated with LEDs.


Figure 7.2: Left and Right Sensor Circuit

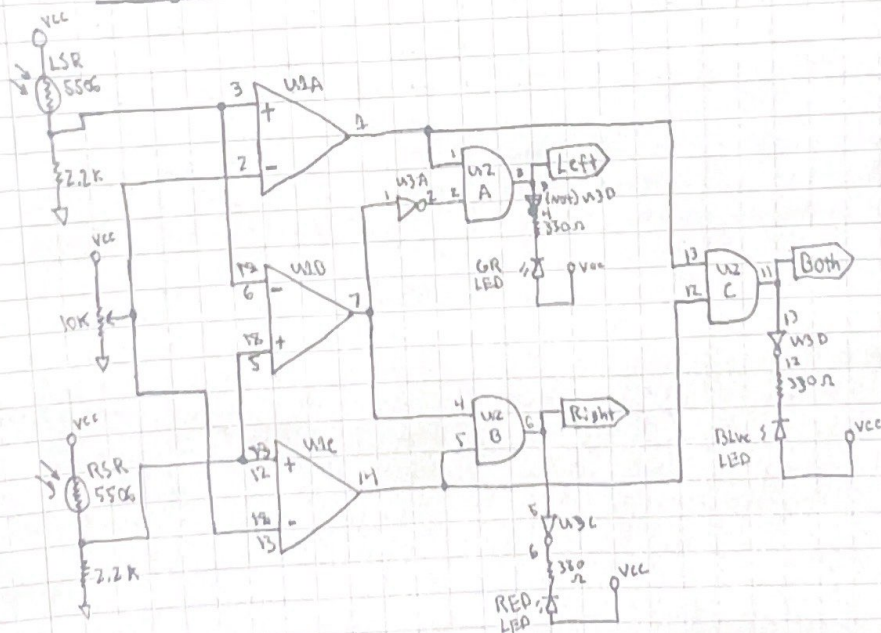

• Before we use these signals we want to gate them to a switch for the 3 independent modes. We can use a 3 state switch to select between Indicate, Turn, or Drive, to gate the Left and Right Inputs; and Drive, to gate Left, Right, and Both Inputs.

Z.C. 12/12/22

Figure 7.3: Mode Toggle Gating Circuit

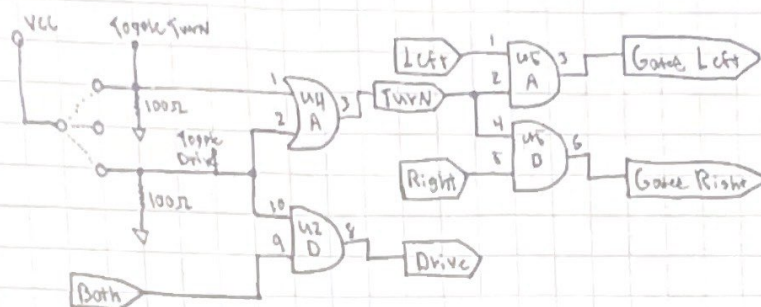

• Let's summarize what we have so far. We have two light sensors that can give us three signals to control our motors: Turn Left (Left side is darker than right side), Turn Right (Right side is darker than left), and Drive forward (Both sides are bright). These control signals are then gated to give us control over our three modes: Indicate (Always on), Turning (Robot will turn), and Drive (Robot will move toward the light).

We need to now look at how we want the motors to move to achieve this kind of motion. With the two track chassis provided this will be a tank steering system.

In other words, To turn Right the Right motor should go in Reverse, ~~the Left~~ while the Left motor continues to go forward; To turn Left the Left motor should go in Reverse while the Right motor goes forward. We have two motors (12V DC) that must go forward in forward and Reverse, so we need 2 separate H-Bridge driver circuits that are isolated. Keep in mind the Optocouplers will be active Low but our current signals are active high, so we will invert the signals before the Opto Couplers.


For now, we will focus on the turning motion and implement forward motion later.

We will use our two input signals (Gate Left and Gate Right) to control our four outputs: Left Motor Forward (LMF), Left Motor Reverse (LMR), Right Motor Forward (RMF), and Right Motor Reverse (RMR). Because of the design of the Left and Right Inputs they will flip-flop or toggle and never be active at the same time. We can then connect Gate Left to Left Motor Reverse and Right Motor Forward. We can connect Gate Right to Right Motor Reverse and Left Motor Forward. Again, this is only to turn the chassis Left and Right we will implement the Drive signal to override the turn controls after displaying the connections to control turning.

Lab 7: Projects

Figure 7.4: Turning Motor Signal Connections

Z.C. 12/12/22

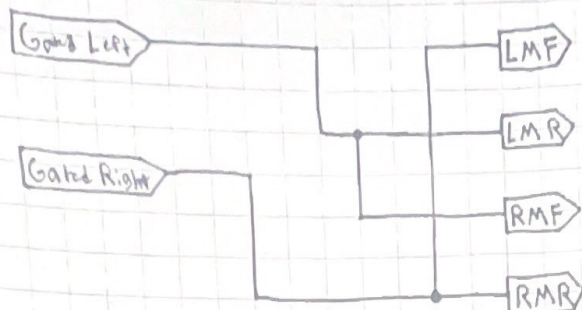

- We can now look at implementing the drive signal to move both motors forward. To do this we will look at how the Drive signal should effect the forward and Reverse signals for both motors.


Forward

When Drive is 0 it should Differ the Left/Right signal. When Drive is 1 the forward signal should be 1.

Table 7.1: Forward Signal Drive Coding Truth Table

Drive(D)	Inputs		out Pins	
	GLeft	GRight	LMF	RMF
0	0	1	1	0
0	1	0	0	1
1	0	1	1	1
1	1	0	1	1
0	0	0	0	0

D or L/R
 $D + L/R$

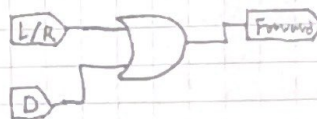
Reverse

When Drive is 0 it should Differ. When L/R is 1 it should be 0 and if L/R is 0 it should Remain 0. When Drive is 1.

Table 7.2: Reverse Signal Drive Coding Truth Table

Drive(D)	GLeft/Right (L/R)	Motor Reverse
0	0	0
0	1	1
1	0	0
1	1	0

$\bar{D} \cdot L/R$

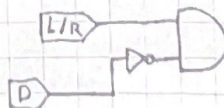


- We can now combine these two gating techniques to have the motor turn when Drive is 0 and move forward when Drive is 1.

ZC.12/12/22

Table 7.3: Left and Right with gate Drive Truth table (Fig 7.5)

Inputs			Outputs			
Drive	GLeft	GRight	LMF	LMR	RMF	RMR
0	0	0	0	0	0	0
0	0	1	1	0	0	1
0	1	0	0	1	1	0
1	0	1	1	0	1	0
1	1	0	1	0	1	0
1	1	1	1	0	1	0

Figure 7.5: Left, Right, and Drive Motor Connections

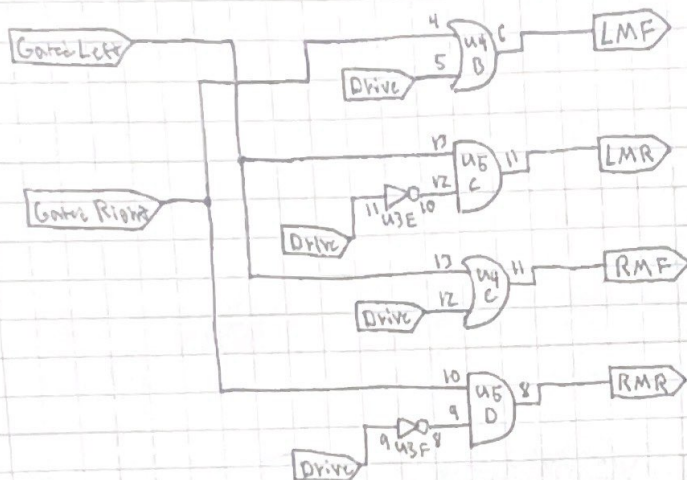

- We now have circuitry that can control the two H-Bridge Drivers in the motor module to turn reverse the motor and drive towards it as well. We will now go over how to connect these signals to two H-Bridge Drivers while providing isolation from the control circuitry.

- H-Bridge Drivers are Opto-Isolation covered in detail on Pg. 39 & 40.
(important current loading update to figures 6.3.12 and 6.3.14)


For the previous figures we inverted the signal and used a Not gate to drive two Optocoupler Inputs. This caused the IOL of that Inversion gate to exceed IOL Max (16mA): $V_{CC} - V_{DIO} = 5V - 2V = 3V$ $3V / 330 = 9.09mA$ $\cdot 2 \text{ inputs} = 18mA$ to prevent this we will use two Not Gates (one for each Input) moving forward.

Lab 7: Projects

- Next we will input our 4 motor control signals into 2 OpAmps (LTV-947) to control our 2 H-Bridge Driver Circuits.

ZC 12/13/22

Figure 7.6: Left and Right Motor OpAmping

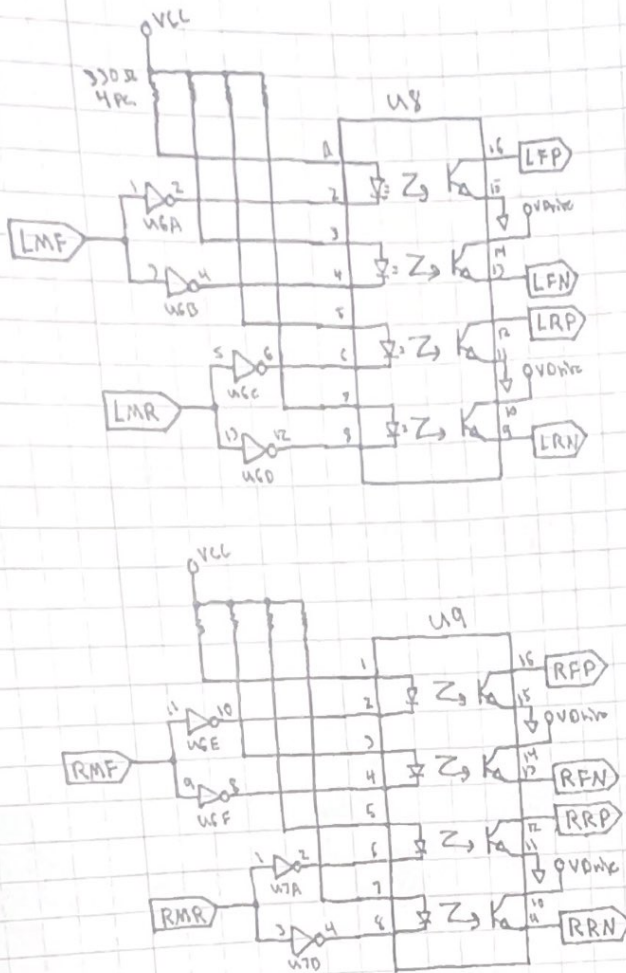


- These 8 output signals will control our 8 MOSFET Gates between the two H-Bridge Drivers. Left Forward P-channel (LFP) and Left Forward N-channel (LFN) to control Left motor forward. Left Reverse P-channel (LRP) and Left Reverse N-channel (LRN) to control Left Motor Reverse. Right Forward P-channel (RFP) and Right Forward N-channel (RFN) for Right Motor forward. Lastly, Right Reverse P-channel (RRP) and Right Reverse N-channel (RRN) for Right Motor Reverse. H-Bridge Drive connections shown in Figure 7.7 Pg. 49.

- We can now assemble our two H-Bridge Drive Circuits. Remember it is important to ensure only the correct MOSFETs switch at once (2 per H-Bridge). If two MOSFETs switch that short the load to ground, high current will pass through the MOSFETs and can damage components.


Z.C. 12/13/22

Figure 7.7: Left and Right H-Bridge Drivers

LEFT

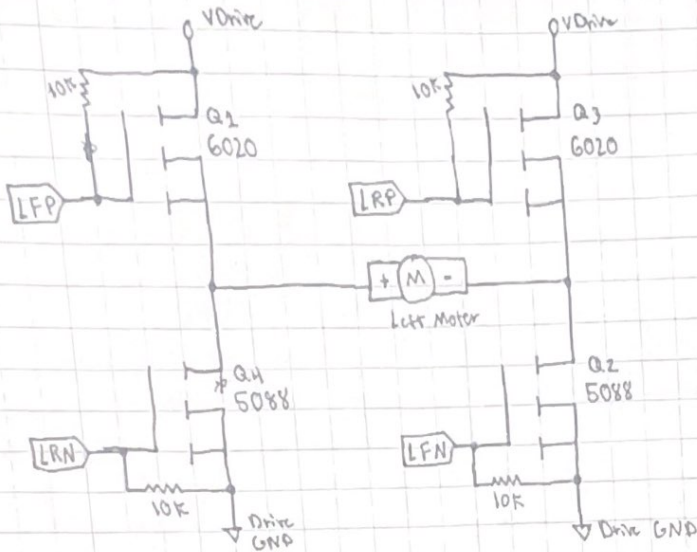

Right

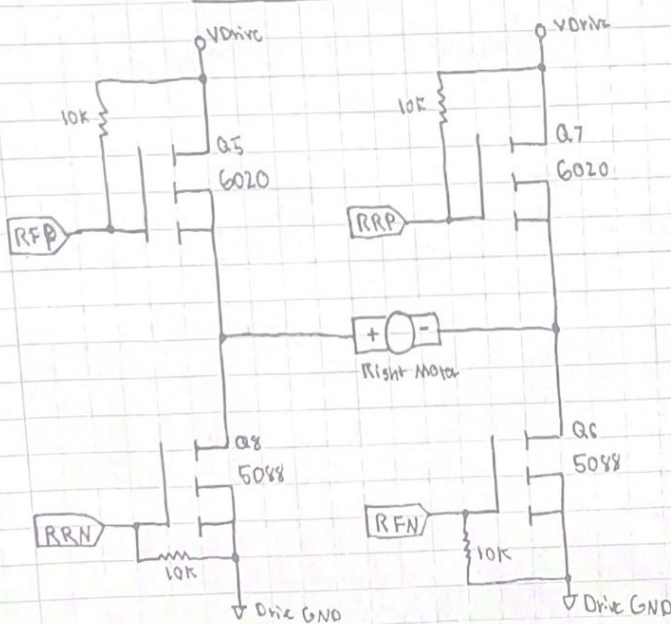

Lab 1: Product

- We now have the full circuit to operate the Robot as intended. Let's take a look at the Integrated Circuits used and the current loading of the whole circuit and each figure.

2.6.12/13/22

17/11/22

ICs used

- U1 - Rail to Rail OP-AMP; MCP6004
- U2 - AND: 7408
- U3 - NOT: 7404
- U4 - OR: 7432
- U5 - AND: 7408
- U6 - NOT: 7404
- U7 - NOT: 7404
- U8 - OpAmp: LTV-847
- U9 - OpAmp: LTV-847

Worst Loading Calculations

Fig 7.2 (Pg. 44)

$I_{OL} = 32\text{mA}$	- U2: Pins 3, 6, 11 - U3: Pins 2, 7, 11
$I_{OH} = 80\text{mA}$	- Same as I_{OL}
$V_{IH} = 5\text{V}$	- All OP-AMP inputs
$V_{IL} = 0\text{V}$	- Same as V_{IH}

Fig 7.3 (Pg. 45)

$I_{OL} = 160\text{mA}$	- U2D: Pin 8
$I_{OH} = 160\text{mA}$	- U2D: Pin 8
$V_{IH} = 5\text{V}$	- U2D: Pin 10 - U4: Pins 1, 2
$V_{IL} = 160\text{mV}$	- Same as V_{IH}

Fig 7.5 (Pg. 47)

$I_{OL} = 32\text{mA}$	- U4: Pins 6, 11 - U5: Pins 8, 11
$I_{OH} = 80\text{mA}$	- Same as I_{OL}
$V_{IH}/V_{IL} = \text{N/A}$	- All voltage inputs are Logic 0

Fig 7.6 (Pg. 48)

$I_{OL} = 9.09\text{mA}$	- U6: Pins 3, 4, 6, 8, 10, 12 - U7: Pins 2, 4
$I_{OH} = 0$	
$V_{IH}/V_{IL} = \text{N/A}$	- Same as Fig 7.5
Sink current = 500mA	- All outputs U6, U7

Figure 2.7 (Pg. 49)

Max current through the MOSFETs is dependent on the Load it is driving. $V_{DS} \cdot I_D / R_{Load} = I_D$. V_{DS} can be up to 12V for the motor but can also function at 5V. $V_{GS} \text{ max} = \pm 20\text{V}$.

Total Circuit (Pg. 44-49)


$I_{OL} = 9.09\text{mA}$	- U6: Pins 3, 4, 6, 8, 10, 12 - U7: Pins 2, 4
$I_{OH} = 160\text{mA}$	- U2: Pin 8
$V_{IH} = 5\text{V}$	- U2: Pin 10 - U4: Pins 1, 2 - All OP-AMP inputs
$f_T \approx 110\text{ns}$	U3A → U2A → U5A → U6C → U6C (excluding OP-AMP and OpAmp)

With the circuit fully designed and tested, let's take a look at the schematic when soldered onto the PCB board. The changes made do not effect the logic or function of the previous circuit. The changes that were made were done in order to minimize the data transfer between Project board and to use the minimal number of components/unused gates per board. Due to the limited space on each Project board, this circuit will be split among three Project board PCBs. The first board will contain the OP-Amp Comparator Sensing circuitry and the mode selection gating. The second board will contain the logic to control the motor Left, Right, and Straight. While the final board will have the dual H-Bridge drivers and Optical Isolation. Let's look at each board and the changes made during assembly.

Project Board 1: Sensing and Gating

This board had the most changes to the schematic. For this section of the circuit we required two Inversions and a single OR gate, to prevent chatty gates when using a 7432 and 7404 we utilized a NAND gate to create OR logic with 3 of the NAND gates and the last as a NOT gate. The final Inversion was to light an indication LED on Low logic. Instead we will use a BJT driver to light the LED on High logic with out overloading current specs. The revised schematic is as follows in fig 7.8. With 4 outputs to Board 2.

Figure 7.8: Project Board 1: Sensing and Gating

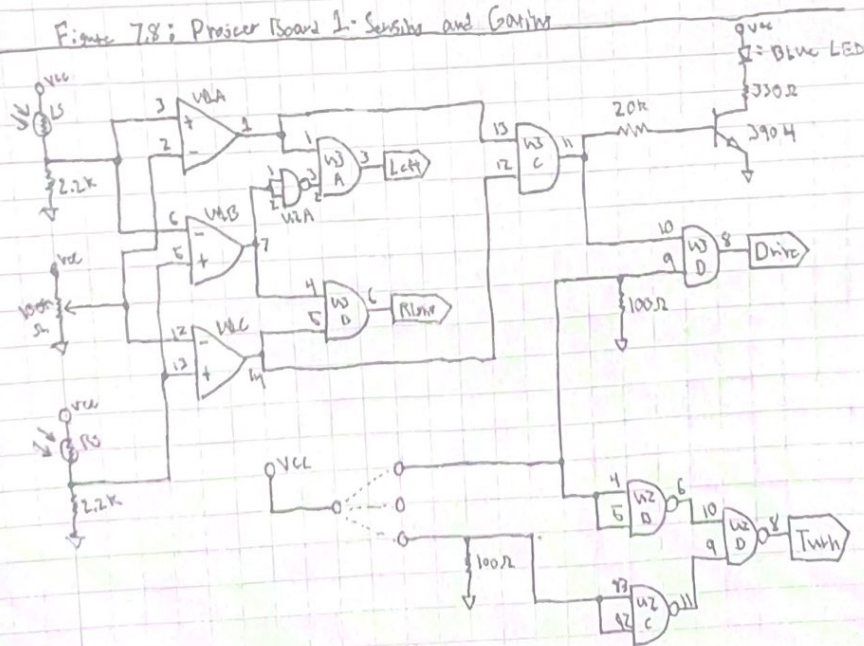

An Attempt was made to regulate

12v In to 5v so the Motors could
run on 12v, while the Logic runs on 5v.

The Opto-Isolation is already in Place. However,

When Attempting we had lots of current drawn
through the Regulator. The Two H-Bridge PCB seems
to be working fine (as of 5/1/23). Next

test should be extra grounding as I believe
there may be grounding issues on the
TTL logic and 12v H-Bridge.

Zoe Christensen

~~Wendy~~

~~Christensen~~

5/1/23